

PAC PCB Layout Guidelines

Power Application Controller™

John Goodrich
Senior Manager, PAC Applications



TABLE OF CONTENTS

APPLICATION NOTE	1
Table of Contents	2
PCB Layout Guidelines	3
1. Ground Connections	4
2. Power Decoupling Capacitors.....	5
3. Gate Drivers	6
4. Analog Inputs	7
About Active-Semi.....	8

PCB LAYOUT GUIDELINES

The PAC52XX family of controllers has a high level of analog integration to make system design much easier for many types of high-voltage control applications. Because of this integration, layout requirements are important for proper operation of the system.


This document provides an overview of the layout guidelines for both high and low-voltage systems using the PAC52XX family of power application controllers.

1. GROUND CONNECTIONS

The ground connection to the IC (IC Ground), the ground connection to the DC-DC (DC-DC Ground), and the ground connection to the motor drive FETs (Power Ground) should be drawn to be isolated from each other. They should only get connected together at the main supply bus capacitor. Please refer to the figure below for illustration.


All PAC52XX device ground pins (VSS, VSSA and VSSP), if available in the IC package should be connected directly to the thermal/ground pad at the bottom of the package.

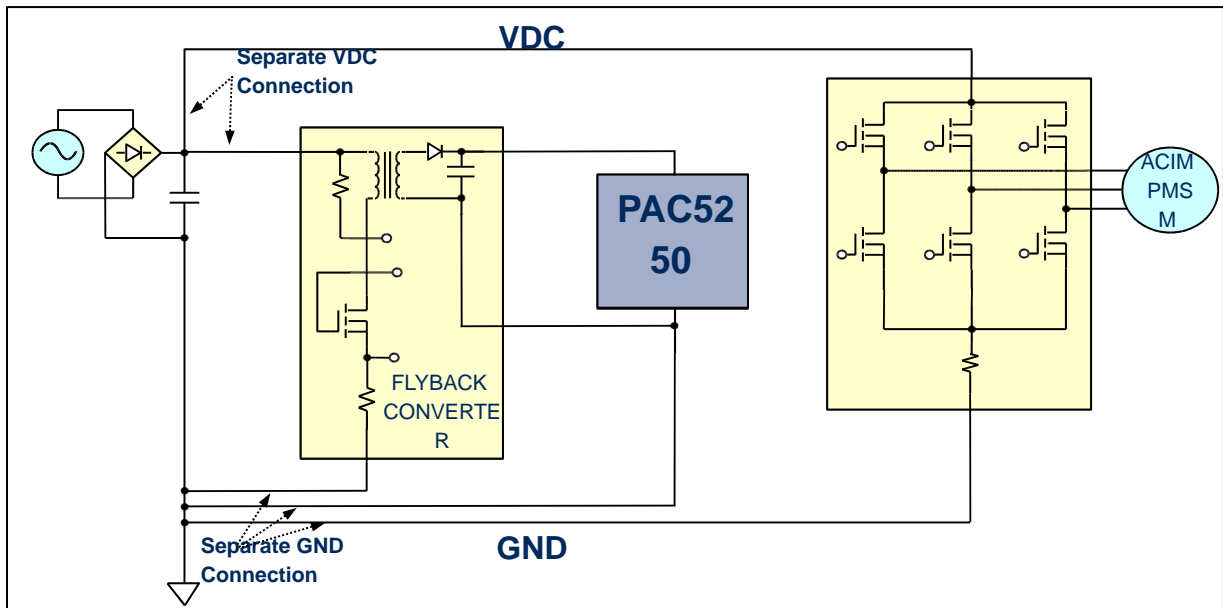The thermal/ground pad at the bottom of the package should have a solid connection with multiple vias to the IC Ground portion of the ground plane on the PCB.



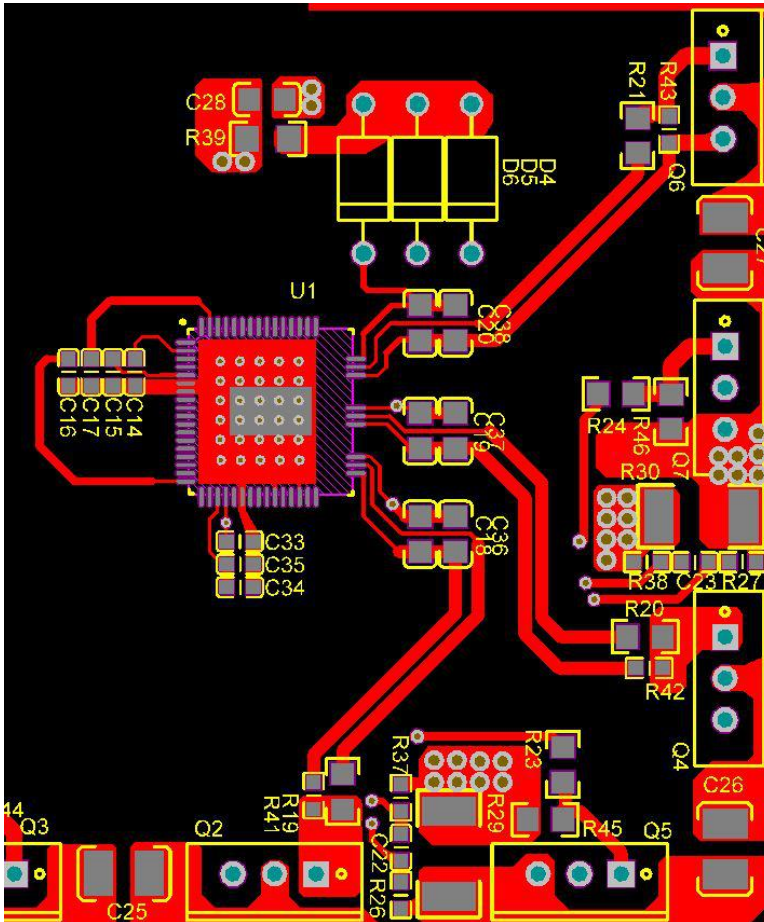2. POWER DECOUPLING CAPACITORS


The decoupling capacitors for VCC18, VCC33, VCCIO, VSYS, VHM, CSM should all be placed as close as possible to the device and routed with the shortest traces possible. Please refer to the following designators in the figure below for illustration on the recommended placement of the decoupling capacitors: C14, C15, C16, C17, C33, C34, and C35.



Decoupling Cap Placement & High-Side Driver Routing

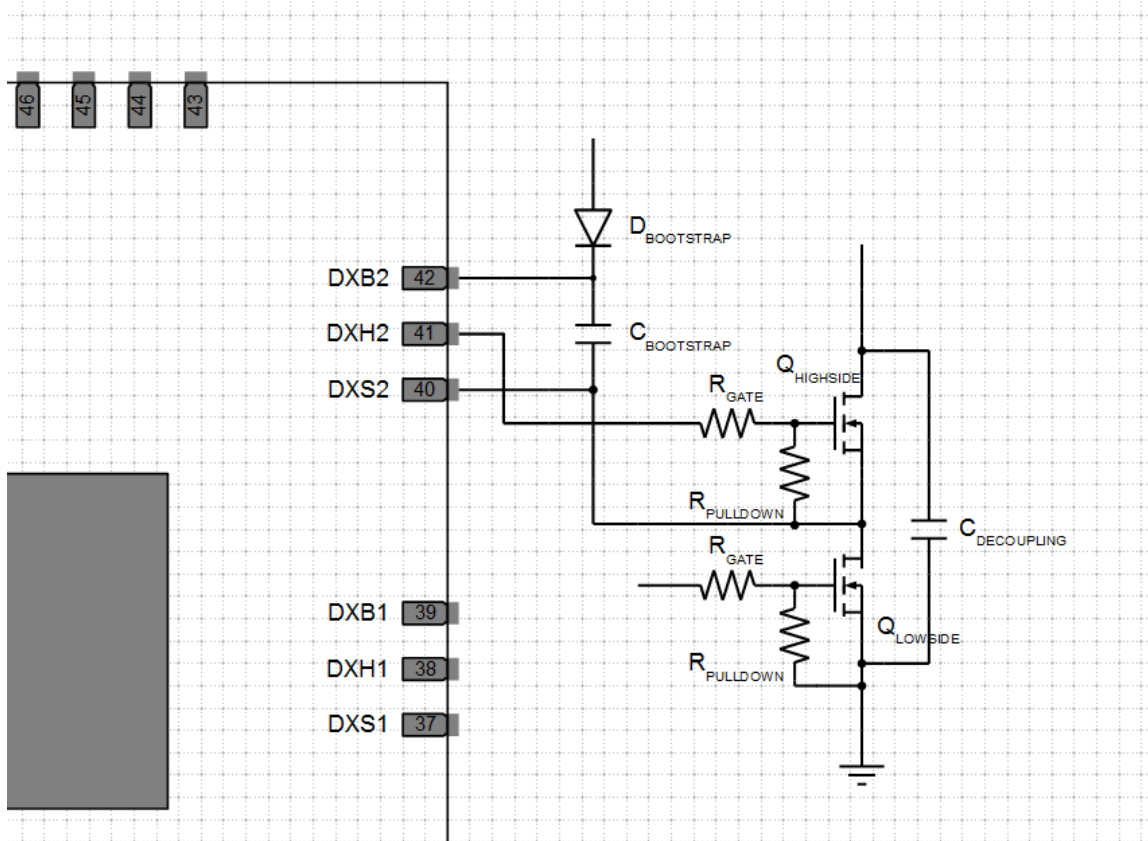3. GATE DRIVERS

Below are the recommendations to follow for the PCB connection to the gate drivers. Please refer to the figure below for reference.



High-Side Gate Driver Schematic

- The high side driver should be fan out to meet IPC-2221A creeping distance recommendations (high voltage designs only).
- The high-side gate driver bootstrap capacitor $C_{\text{BOOTSTRAP}}$ and boot-strap diode $D_{\text{BOOTSTRAP}}$ should be placed as close as possible to the device.
- Both High-Side and Low-Side gate drive resistor R_{GATE} and R_{PULLDOWN} should be placed as close as possible to the Power FET.
- The Half-Bridge decoupling capacitor $C_{\text{DECOUPLING}}$ should be placed as close as possible to Q_{HIGHSIDE} and Q_{LOWSIDE}

4. ANALOG INPUTS

RC filter or filter capacitors for the AIO analog inputs should be placed as close as possible to the device, with ground routing as short as possible.

ABOUT ACTIVE-SEMI

Active-Semi, Inc. headquartered in Dallas, TX is a leading innovative semiconductor company with proven power management, analog and mixed-signal products for end-applications that require power conversion (AC/DC, DC/DC, DC/AC, PFC, etc.), motor drivers and control and LED drivers and control along with ARM microcontroller for system development.

Active-Semi's latest family of Power Application Controller (PAC)[™] ICs offer high-level of integration with 32-bit ARM Cortex M0, along with configurable power management peripherals, configurable analog front-end with high-precision, high-speed data converters, single-ended and differential PGAs, integrated low-voltage and high-voltage gate drives. PAC IC offers unprecedented flexibility and ease in the systems design of various end-applications such as Wireless Power Transmitters, Motor drives, UPS, Solar Inverters and LED lighting, etc. that require a microcontroller, power conversion, analog sensing, high-voltage gate drives, open-drain outputs, analog & digital general purpose IO, as well as support for wired and wireless communication. More information and samples can be obtained from <http://www.active-semi.com> or by emailing marketing@active-semi.com

Active-Semi shipped its 1 Billionth IC in 2012, and has over 120 in patents awarded and pending approval.

LEGAL INFORMATION & DISCLAIMER

Copyright © 2012-2013 Active-Semi, Inc. All rights reserved. All information provided in this document is subject to legal disclaimers.

Active-Semi reserves the right to modify its products, circuitry or product specifications without notice. Active-Semi products are not intended, designed, warranted or authorized for use as critical components in life-support, life-critical or safety-critical devices, systems, or equipment, nor in applications where failure or malfunction of any Active-Semi product can reasonably be expected to result in personal injury, death or severe property or environmental damage. Active-Semi accepts no liability for inclusion and/or use of its products in such equipment or applications. Active-Semi does not assume any liability arising out of the use of any product, circuit, or any information described in this document. No license, express, implied or otherwise, is granted under any patents, copyrights or other intellectual property rights of Active-Semi or others. Active-Semi assumes no liability for any infringement of the intellectual property rights or other rights of third parties which would result from the use of information contained herein. Customers should evaluate each product to make sure that it is suitable for their applications. Customers are responsible for the design, testing, and operation of their applications and products using Active-Semi products. Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products. All products are sold subject to Active-Semi's terms and conditions of sale supplied at the time of order acknowledgment. Exportation of any Active-Semi product may be subject to export control laws.

Active-Semi[™], Active-Semi logo, Solutions for Sustainability[™], Power Application Controller[™], Micro Application Controller[™], Multi-Mode Power Manager[™], Configurable Analog Front End[™], and Application Specific Power Drivers[™] are trademarks of Active-Semi, I. ARM[®] is a registered trademark and Cortex[™] is a trademark of ARM Limited. All referenced brands and trademarks are the property of their respective owners.